

# L76-LB

# Reference Design

**GNSS Module Series**

Rev. L76-LB\_Reference\_Design\_V1.0

Date: 2019-05-13

Status: Released



**Our aim is to provide customers with timely and comprehensive service. For any assistance, please contact our company headquarters:**

**Quectel Wireless Solutions Co., Ltd.**

7<sup>th</sup> Floor, Hongye Building, No.1801 Hongmei Road, Xuhui District, Shanghai 200233, China

Tel: +86 21 5108 6236

Email: [info@quectel.com](mailto:info@quectel.com)

**Or our local office. For more information, please visit:**

<http://www.quectel.com/support/sales.htm>

**For technical support, or to report documentation errors, please visit:**

<http://www.quectel.com/support/technical.htm>

Or email to: [support@quectel.com](mailto:support@quectel.com)

## **GENERAL NOTES**

QUECTEL OFFERS THE INFORMATION AS A SERVICE TO ITS CUSTOMERS. THE INFORMATION PROVIDED IS BASED UPON CUSTOMERS' REQUIREMENTS. QUECTEL MAKES EVERY EFFORT TO ENSURE THE QUALITY OF THE INFORMATION IT MAKES AVAILABLE. QUECTEL DOES NOT MAKE ANY WARRANTY AS TO THE INFORMATION CONTAINED HEREIN, AND DOES NOT ACCEPT ANY LIABILITY FOR ANY INJURY, LOSS OR DAMAGE OF ANY KIND INCURRED BY USE OF OR RELIANCE UPON THE INFORMATION. ALL INFORMATION SUPPLIED HEREIN IS SUBJECT TO CHANGE WITHOUT PRIOR NOTICE.

## **COPYRIGHT**

THE INFORMATION CONTAINED HERE IS PROPRIETARY TECHNICAL INFORMATION OF QUECTEL WIRELESS SOLUTIONS CO., LTD. TRANSMITTING, REPRODUCTION, DISSEMINATION AND EDITING OF THIS DOCUMENT AS WELL AS UTILIZATION OF THE CONTENT ARE FORBIDDEN WITHOUT PERMISSION. OFFENDERS WILL BE HELD LIABLE FOR PAYMENT OF DAMAGES. ALL RIGHTS ARE RESERVED IN THE EVENT OF A PATENT GRANT OR REGISTRATION OF A UTILITY MODEL OR DESIGN.

***Copyright © Quectel Wireless Solutions Co., Ltd. 2019. All rights reserved.***

# About the Document

## History

Revision	Date	Author	Description
1.0	2019-05-13	Jaden XIANG/ Gene LI	Initial

---

## Contents

About the Document.....	2
Contents .....	3
<b>1 Reference Design.....</b>	<b>4</b>
1.1. Introduction .....	4
1.2. Schematics .....	4

# 1 Reference Design

## 1.1. Introduction

This document provides the reference design for Quectel L76-LB module.


## 1.2. Schematics

The schematics illustrated in the following pages are provided for your reference only.


# 3.3V Power Supply and UART Circuit

If the MCU power supply is 3.3V, please refer to the reference designs as below.

## Customer's MCU

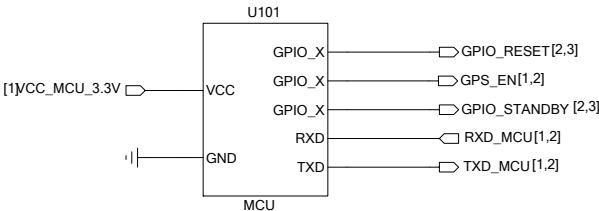


## UART Circuit

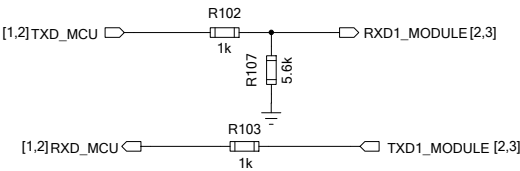

**Note:**  
R102, R103, R107 are designed for 3.3V MCU level match.

## Power Management Circuit (Optional)

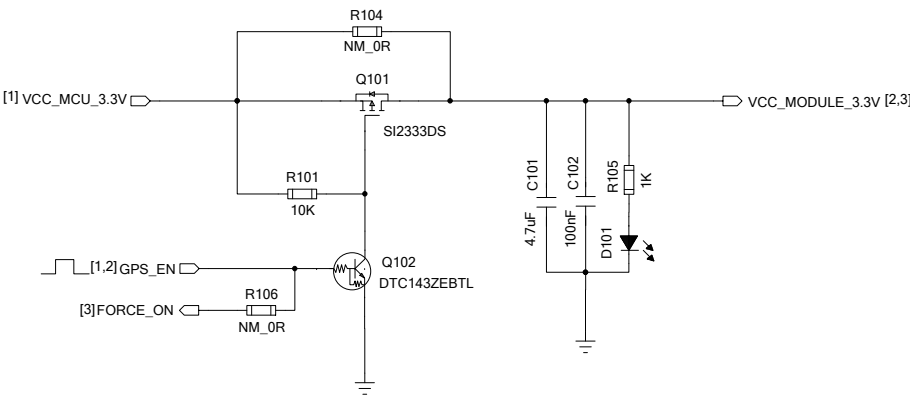

- Notes:**  
There are two ways to enter into backup mode and return to full on mode.
1. Send command "\$PMTK225,4\*2F" to enter into backup mode constantly. The only way to wake up the module is by pulling FORCE\_ON pin high. In such case, Q101, Q102, R101 are not mounted; R104 and R106 are 0Ω
  2. Cut off the power of VCC and keep V\_BCKP powered to enter into backup mode from full on mode. As soon as the VCC pin is powered, the module will enter into full on mode immediately. In such case, Q101, Q102, R101 are mounted; R104 and R106 are not mounted.


## Quectel Wireless Solutions

DRAWN BY Jaden	PROJECT L76-LB	TITLE Reference Design
CHECKED BY Brooke	SIZE A2	VER 1.0
SHEET	1 OF 4	DATE 2019/05/13


# 5.0V Power Supply and UART Circuit

If the MCU power supply is 5.0V, please refer to the reference designs as below.


## Customer's MCU

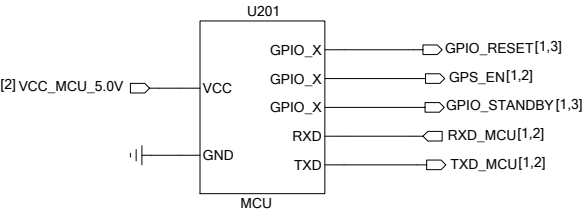

## LDO Circuit

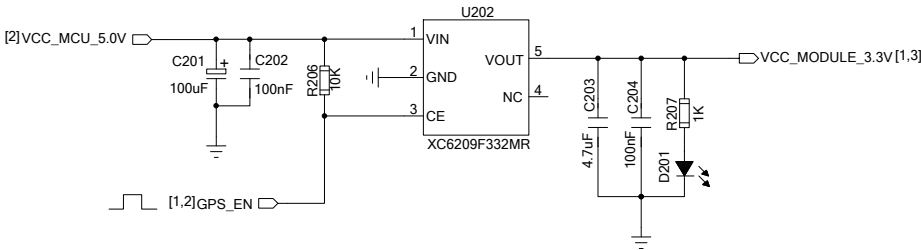

## Level Shifting for UART

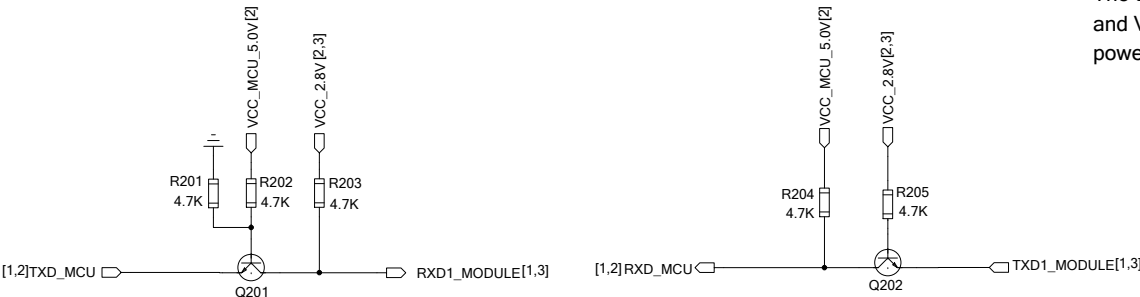


Note:  
The transistor circuit will shift voltage level between VCC\_MCU\_5.0V and VCC\_2.8V, and block the current leakage when the module is powered on/off.

### Quectel Wireless Solutions


DRAWN BY Jaden	PROJECT L76-LB	TITLE Reference Design
CHECKED BY Brooke	SIZE A2	VER 1.0
SHEET	2 OF 4	DATE 2019/05/13

# Module Interface

## Module Interface

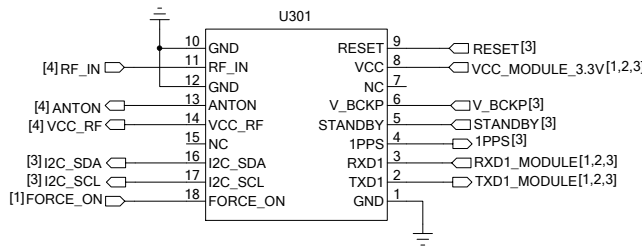


## Test Points

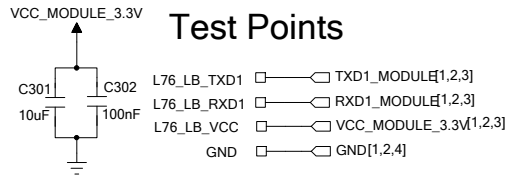


- Notes:
1. UART interface is used for NMEA output, PMTK/PQ commands input and firmware upgrade.
  2. The test points are reserved for debugging the GNSS module.

## Charge Circuit for RTC Logic

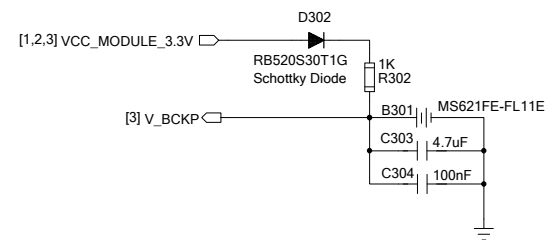


Note:  
V\_BCKP is designed to supply power for L76-LB RTC logic circuit when VCC\_MODULE\_3.3V is powered off.

## I2C Circuit for L76-LB

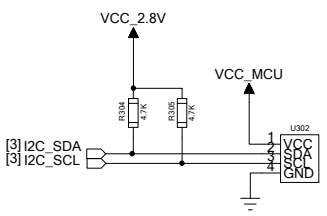


- Notes:
1. In L76-LB, I2C\_SDA/I2C\_SCL should be pulled up to 2.8V via an external pull-up resistor.
  2. The voltage threshold of I2C is 2.8V. If the system voltage does not conform to it, a level shifter circuit must be used.

## Indicating Circuit

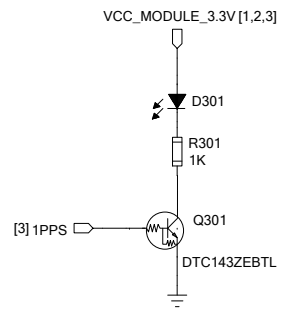


Note:  
The 1PPS indicator will blink at 1Hz frequency after the module fixes position.

## Reset Circuit

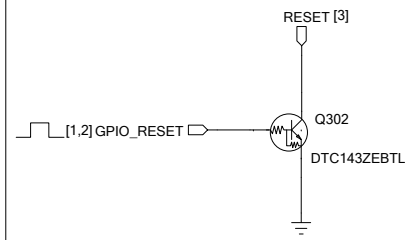

- Notes:
1. If the reset function is unused, RESET pin can be connected to the VCC directly.
  2. RESET has been pulled up internally.

## Standby Circuit

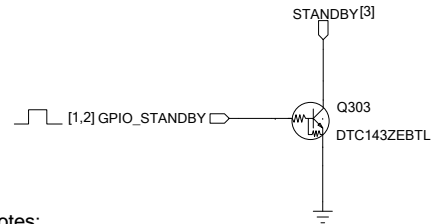

- Notes:
1. STANDBY has been pulled up internally.
  2. Enter into standby mode: change STANDBY pin from high to low level.
  3. Exit from standby mode: change STANDBY pin from low to high level.
- For more details, please refer to *Quectel\_L76-LB\_Hardware\_Design*.


## Quectel Wireless Solutions

DRAWN BY Jaden	PROJECT L76-LB	TITLE Reference Design
CHECKED BY Brooke	SIZE A2	VER 1.0
SHEET	3 OF 4	DATE 2019/05/13



# Antenna Interface

## Active Antenna

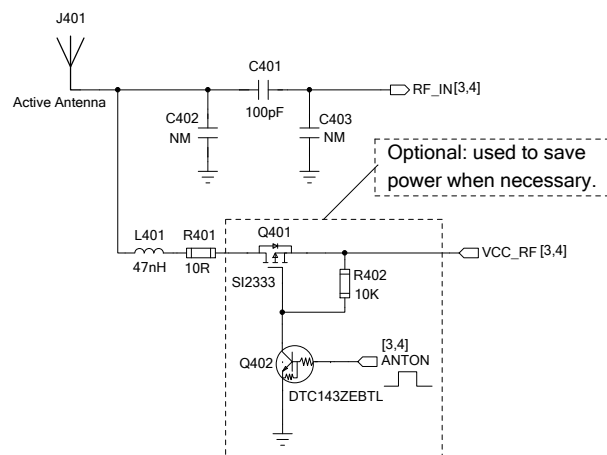


### Notes:

1. Pi type circuit (C401, C402, C403) is reserved for impedance matching for antenna. By default, C402 and C403 are not mounted; C401 is 100pF.
2. VCC\_RF can be used as power supply for active antenna. Its typical value is 3.3V, and the voltage ranges from 2.8V to 4.3V (VCC\_RF=VCC). If it does not meet the requirement of the active antenna, an external LDO could be used.
3. The voltage level of ANTEN will be pulled down in standby mode.
4. If the L76-LB module never enters into standby mode in the design, the ANTEN pin should be kept floating.
5. Impedance of RF trace should be controlled as 50Ω and the trace length should be kept as short as possible.

For more details, please refer to *Quectel\_L76-LB\_Hardware\_Design*.

## Passive Antenna

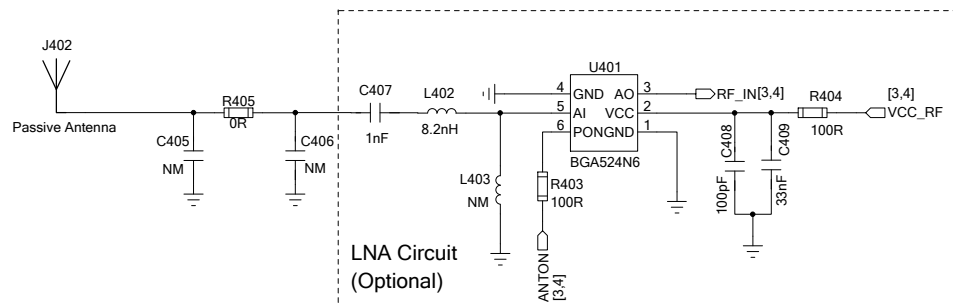

### Notes:

1. Pi type circuit (R405, C405, C406) is reserved for impedance matching for antenna. By default, C405 and C406 are not mounted; R405 is 0Ω.
2. If an external LNA is added between passive antenna and L76-LB module, the total sensitivity will be improved, which is beneficial for TTFF improvement.
3. One typical reference circuit with BGA524N6 is given in the left figure. Here, C407, L402 and L403 form a reserved matching circuit for the LNA BGA524N6. By default, C407 is 1nF; L402 is 8.2nH; and L403 is not mounted.
4. VCC\_RF can be used as power supply for LNA. Its voltage range is from 2.8V to 4.3V, and its typical value is 3.3V (VCC\_RF=VCC)
5. ANTEN is an optional pin which can be used to control the enable pin of an external LNA. If ANTEN function is not used, please connect the LNA\_EN pin (LNA ENABLE) to VCC to keep LNA always on.
6. Impedance of RF trace should be controlled as 50Ω and the trace length should be kept as short as possible.

For more details, please refer to *Quectel\_L76-LB\_Hardware\_Design*.

### Quectel Wireless Solutions

DRAWN BY Jaden	PROJECT L76-LB	TITLE Reference Design
CHECKED BY Brooke	SIZE A2	VER 1.0
SHEET	4 OF 4	DATE 2019/05/13